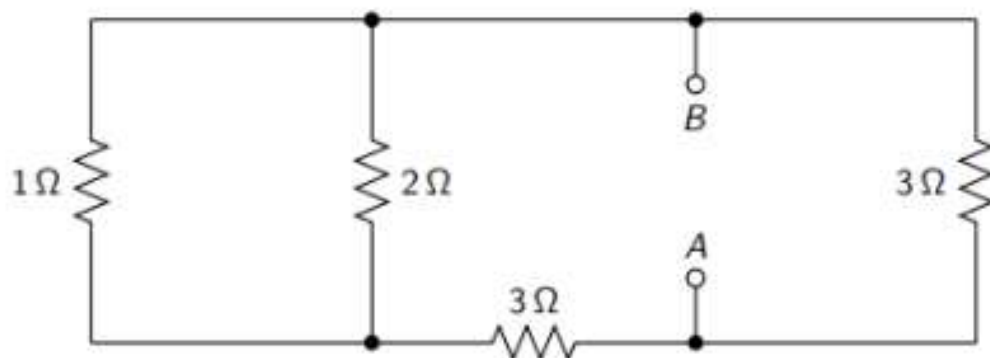


Question 1

Problem: find the equivalent resistance R_{eq} between terminals A and B .




Your answer

Question 2: KCL

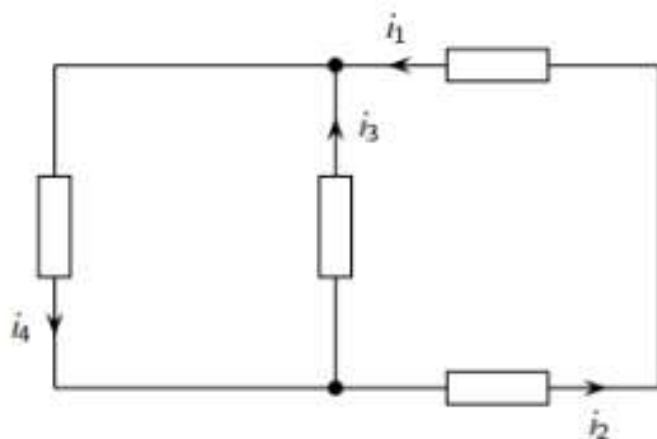Problem: find i_1 , i_3 .

Data: $i_2 = 3\text{ A}$, $i_4 = 1\text{ A}$



Your answer

3) Circuit Design Question *

I want to create a circuit that has a 48W motor and a 0.018 W LED light that turns on at the same time. The light has a maximum current of 0.01A and the motor runs under a maximum Voltage rating of 24V. I only have a 36 volt battery, but I have access to as many resistors as I need.

Create a circuit that allows the light and motor to get their individual power outputs without breaking (48W for the motor, 0.018W for the light).

